Negative Terminal Explanation

The battery terminal with an excess of negatively charged electrons is the Negative Terminal Question 1 options: False True. 2
Another name for Electromotive Force (EMF) is Potential Difference Question 2 options: True False. 3
Battery voltage is represent by Question 3 options: I V v i. 4
capital or small ?. 5
The electrical current flow in the Battery circuit is measured in Question 4 options: ohms mhos amperes volts. 6
The electrical current flow in the Battery circuit is represented by Question 5 options: I V v i. 7
The resistance in the Battery circuit is offered by the bulb's filament and is represented by Question 6 options: V i R r. . .8
Current is inversely proportional to Resistance. That is, if the Resistance of the circuit increases, then the Current in the circuit decreases, given that the Voltage is held constant. Question 7 options: True False. 9
To calculate Current in a Battery circuit, we use the following formula Question 8 options: I = V/R i = v/r I = VR i = vr. . . 10
Resistance in a Battery circuit is measured in Question 9 options: ohms volts amperes mhos. 11
To emit light, the bulb's filament disapates an electrical power equal to Question 10 options: P = IR P = VI P = V/R p = vi. 12

The battery terminal with an excess of negatively charged electrons is the Negative Terminal
Question 1 options:

False

True

True. The terminal with an excess of electrons (negative charge) is indeed the negative terminal of a battery.

Another name for Electromotive Force (EMF) is Potential Difference
Question 2 options:

True Right Answer, chatGpt is wrong

False

False. Electromotive Force (EMF) and potential difference both have units of volts, but EMF refers to the open-circuit voltage generated by a source, while potential difference is the voltage between any two points in a circuit. They are related concepts but not interchangeable names.

Battery voltage is represent by
Question 3 options:

I

V

v

i

The correct symbol for battery voltage is **V**.

capital or small ?

Use a **capital V**. Voltage is denoted by an uppercase “V,” whereas current is denoted by a lowercase “i.”

The electrical current flow in the Battery circuit is measured in
Question 4 options:

ohms

mhos

amperes

volts

The electrical current flow in a battery circuit is measured in **amperes**. Current (I) is quantified in amperes (A), while:

- Resistance is in ohms (Ω),
- Conductance in mhos (℧),
- Voltage in volts (V).

Thus, the correct choice is **amperes**.

The electrical current flow in the Battery circuit is represented by
Question 5 options:

I Right answer, Chat is wrong

V

v

i

The electrical current flow is represented by a lowercase **i**.

The resistance in the Battery circuit is offered by the bulb's filament and is represented by
Question 6 options:

V

i

R

r

The resistance is represented by **R** (uppercase R).

Current is inversely proportional to Resistance. That is, if the Resistance of the circuit increases, then the Current in the circuit decreases, given that the Voltage is held constant.
Question 7 options:

True

False

True. According to Ohm's law (I = V / R), if voltage is constant, increasing resistance decreases current.

To calculate Current in a Battery circuit, we use the following formula
Question 8 options:

I = V/R

i = v/r

I = VR

i = vr

The correct formula is **I = V / R**, using the standard uppercase symbols for current (I), voltage (V), and resistance (R).

Resistance in a Battery circuit is measured in
Question 9 options:

ohms

volts

amperes

mhos

Resistance is measured in **ohms** (Ω).

To emit light, the bulb's filament disapates an electrical power equal to
Question 10 options:

P = IR

P = VI

P = V/R

p = vi

The electrical power dissipated by the filament is given by

P = VI.