
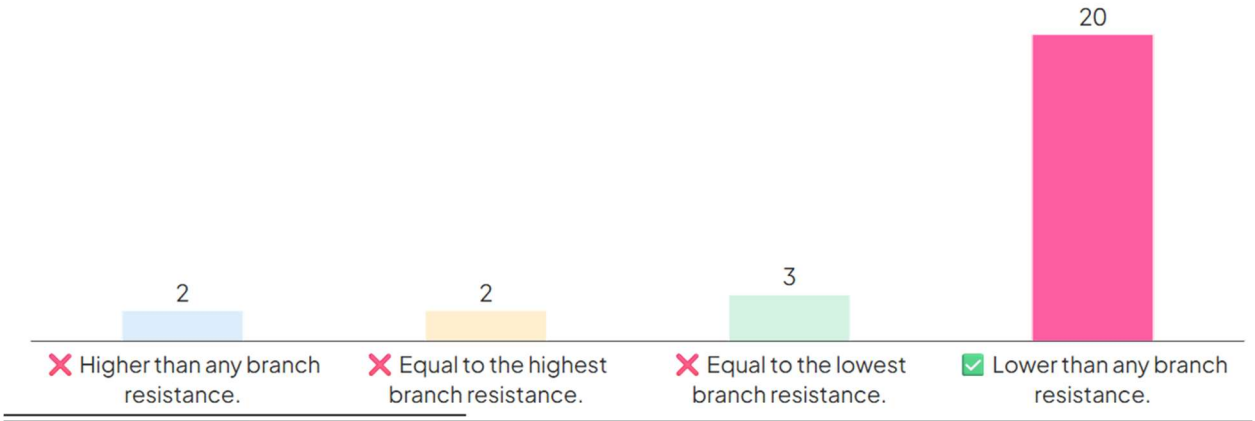
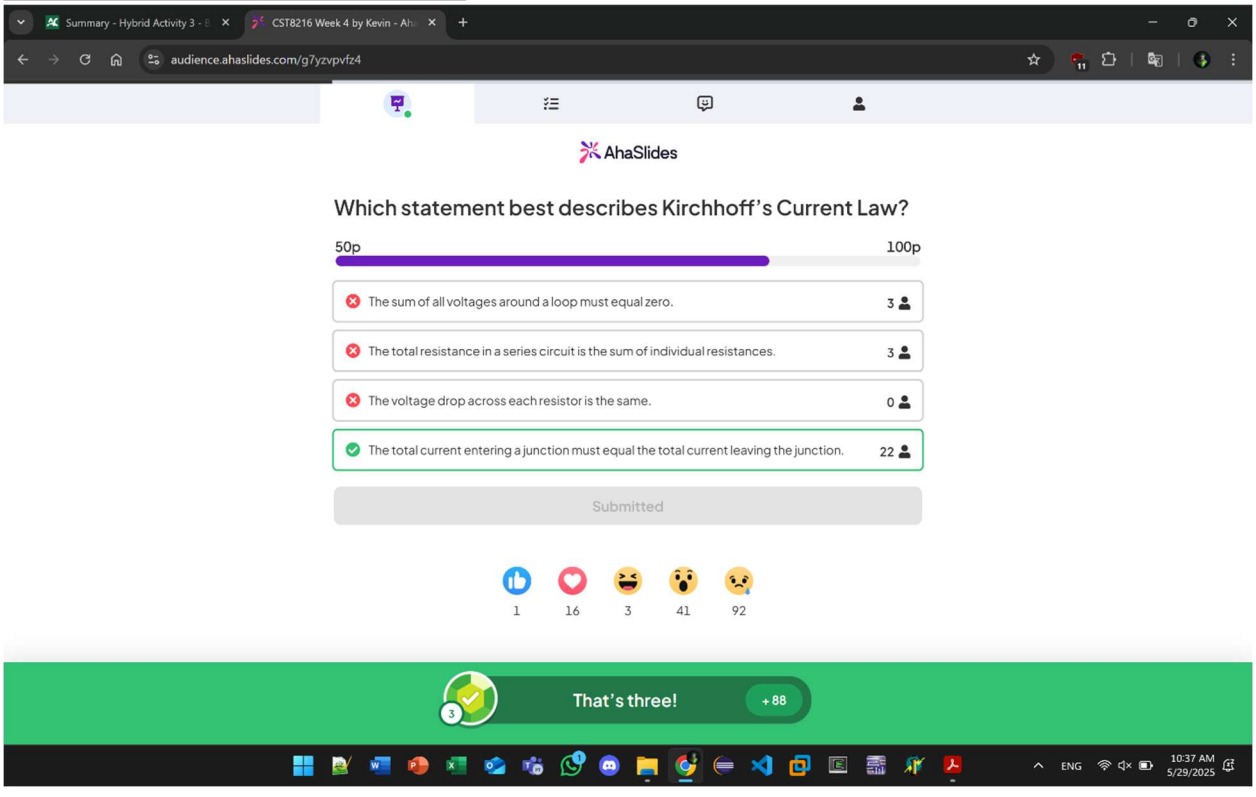
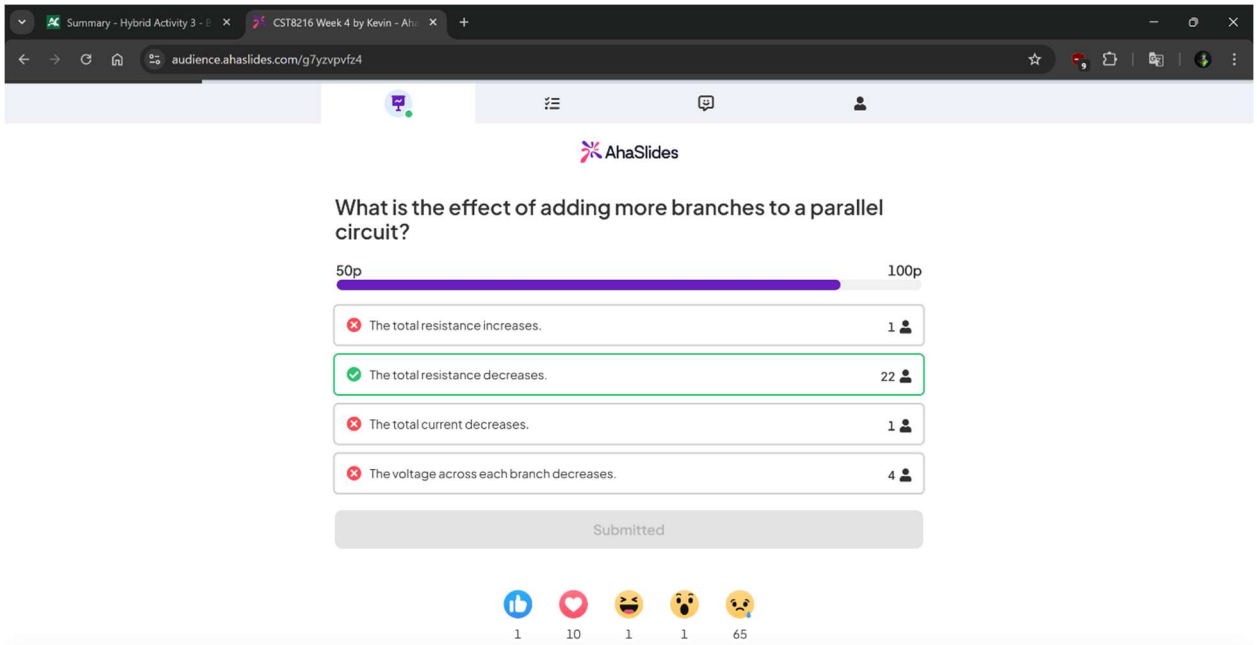
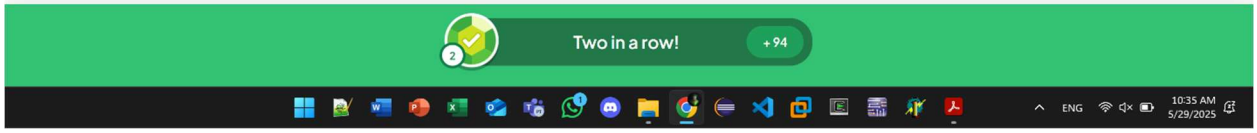
How is the total resistance in a parallel circuit generally compared to the individual branch resistances?



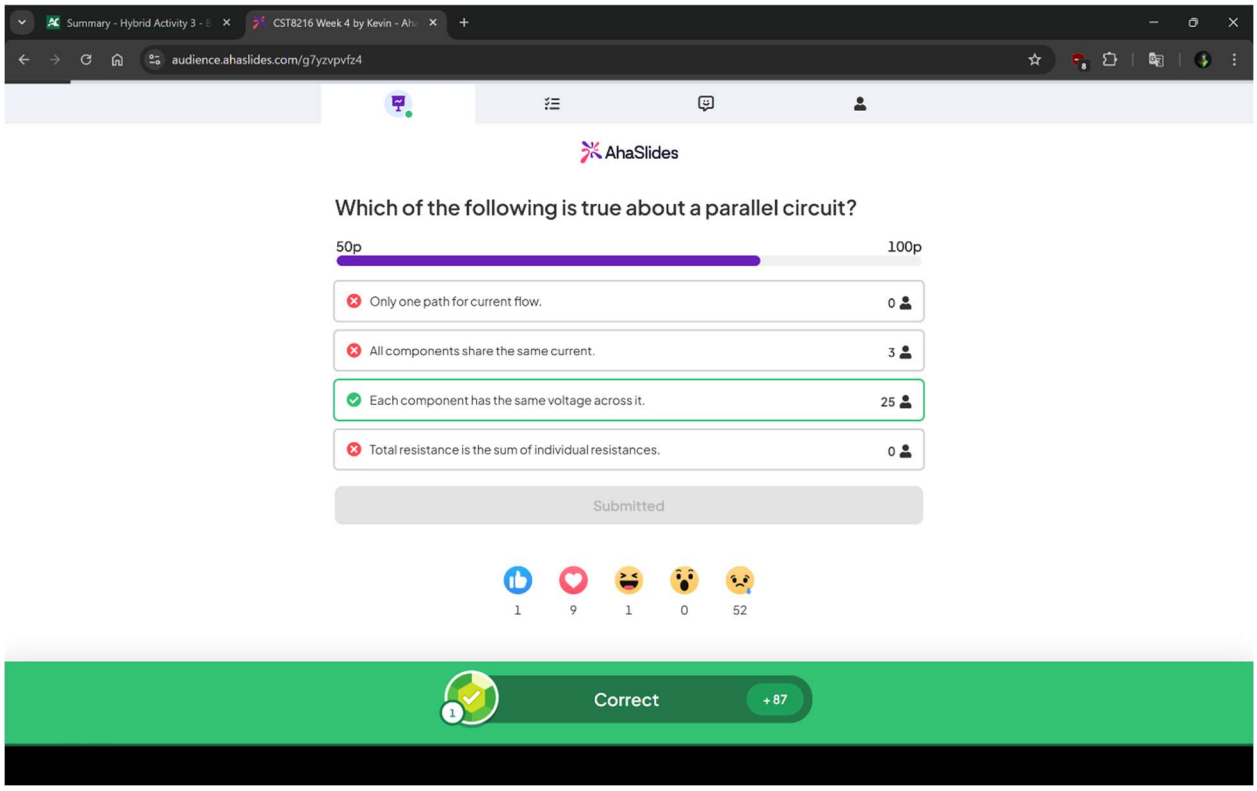

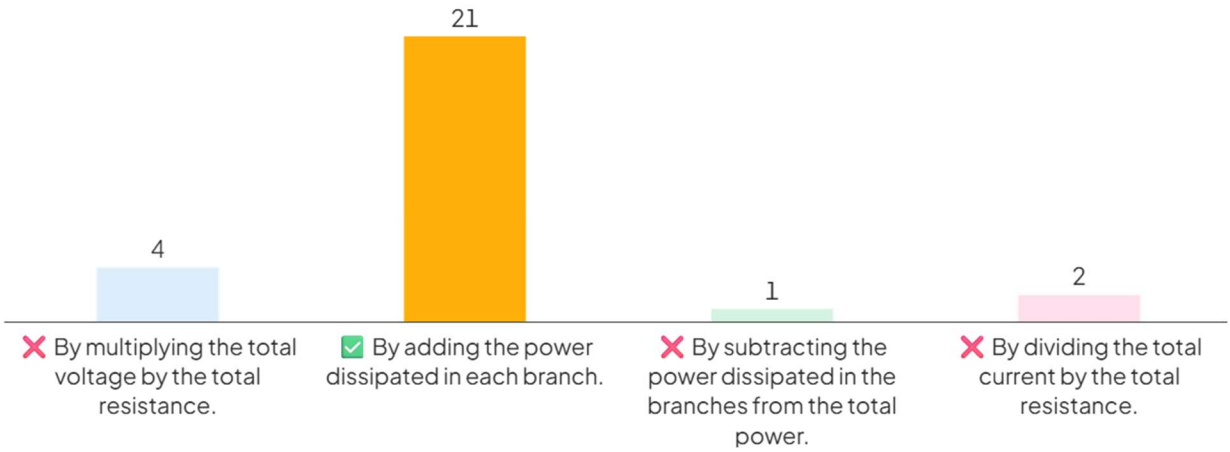

Summary - Hybrid Activity 3 -
CST8216 Week 4 by Kevin - Aha
audience.ahaslides.com/g7yzvpvfz4
AhaSlides
What is the effect of adding more branches to a parallel circuit?
50p
100p
The total resistance increases. 1
The total resistance decreases. 22
The total current decreases. 1
The voltage across each branch decreases. 4
Submitted
1
10
1
1
65

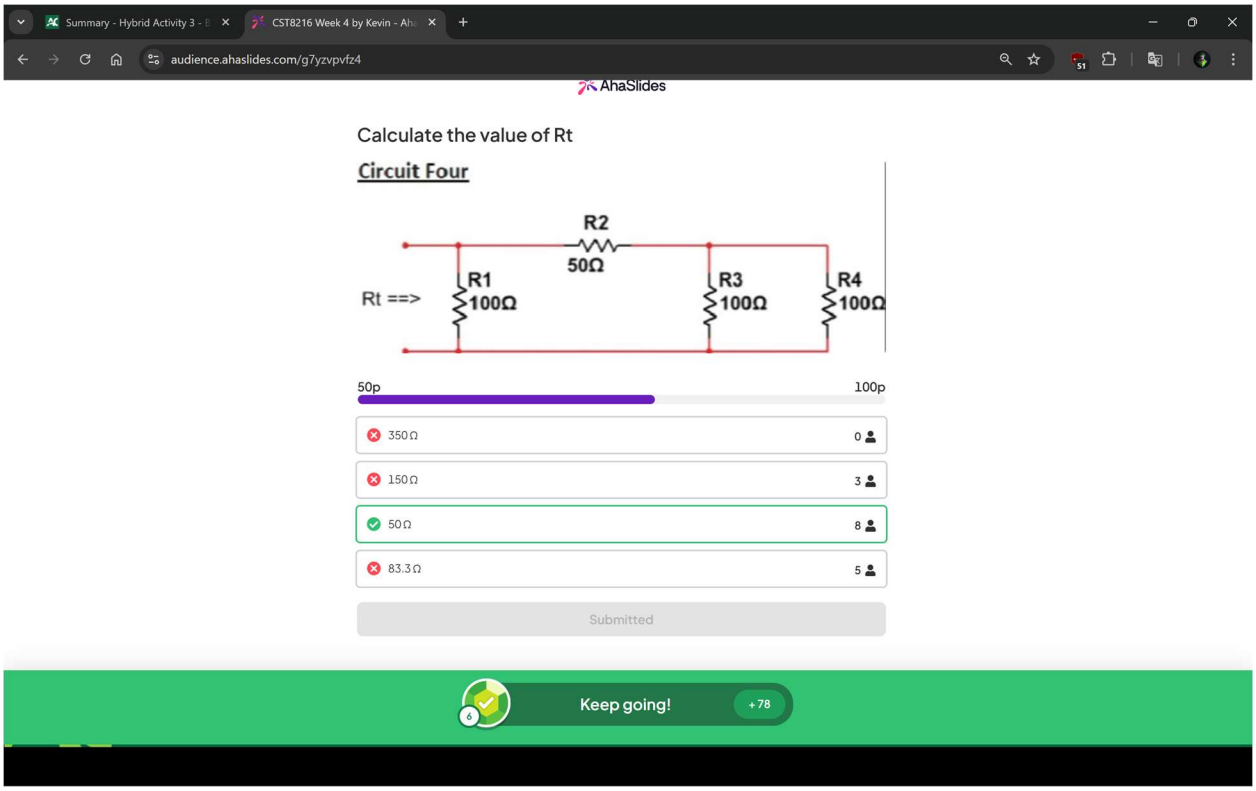

2
Two in a row!
+94
ENG
10:35 AM
5/29/2025


Summary - Hybrid Activity 3 -
CST8216 Week 4 by Kevin - Aha
audience.ahaslides.com/g7yzvpvfz4
AhaSlides
Which of the following is true about a parallel circuit?
50p
100p
Only one path for current flow. 0
All components share the same current. 3
Each component has the same voltage across it. 25
Total resistance is the sum of individual resistances. 0
Submitted
1
9
1
0
52

1
Correct
+87

How is the total power in a parallel circuit calculated?






Summary - Hybrid Activity 3 - B | CST8216 Week 4 by Kevin - Aha | audience.ahaslides.com/g7yzvpvfz4

AhaSlides

Calculate the value of Rt

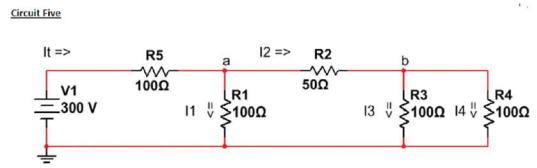

50p 100p

✗ 350 Ω	1
✓ 150 Ω	18
✗ 300 Ω	0
✗ 33.3 Ω	1


Submitted

7 Awesome! +92

Summary - Hybrid Activity 3 - B | CST8216 Week 4 by Kevin - Aha | audience.ahaslides.com/g7yzvpvfz4

AhaSlides

Calculate the value of Va

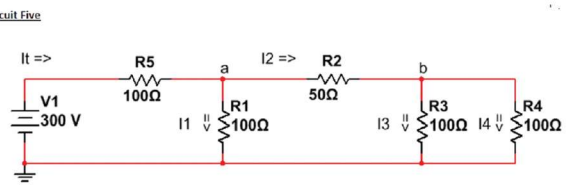

50p 100p

✗ 200 V	2
✓ 100 V	15
✗ 50 V	0
✗ 150 V	1

8 Good job! +79


Summary - Hybrid Activity 3 - B | CST8216 Week 4 by Kevin - Aha

audience.ahaslides.com/g7yzvpvfz4

AhaSlides

Calculate the value of Vb

Circuit Five

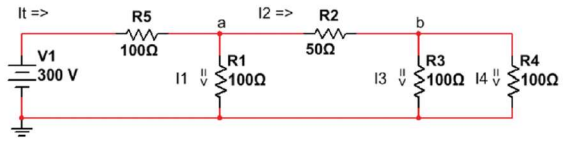

50p 100p

✗ 200 V	2
✗ 100 V	2
✓ 50 V	12
✗ 150 V	2


Oh no, streak lost! +0

Summary - Hybrid Activity 3 - B | CST8216 Week 4 by Kevin - Aha

audience.ahaslides.com/g7yzvpvfz4

AhaSlides

Calculate the value of Rt

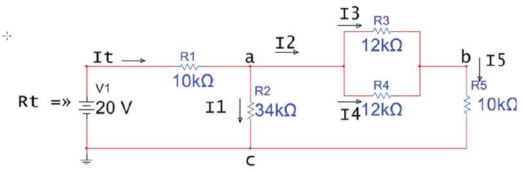


50p 100p


✗ 60 kΩ	1
✗ 10.88 Ω	0
✓ 20.88 kΩ	14
✗ 10.11 kΩ	0

Correct +84

AhaSlides

Calculate the value of Va

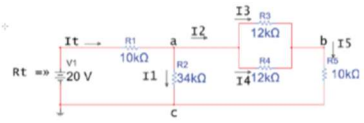

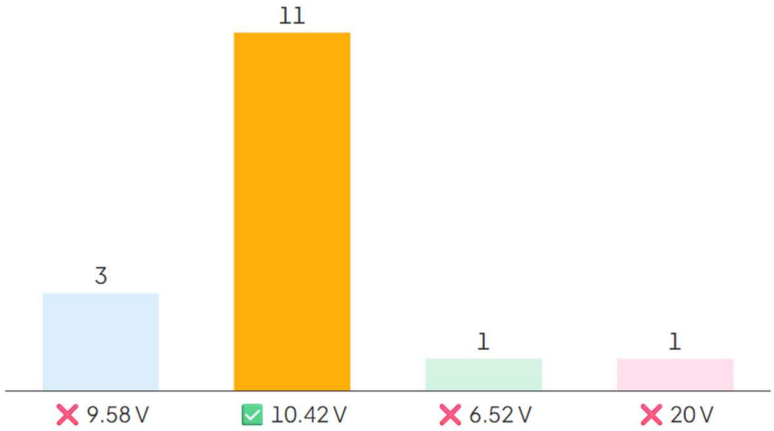


Summary - Hybrid Activity 3 - E | CST8216 Week 4 by Kevin - Aha

audience.ahaslides.com/g7yzvpvfz4

AhaSlides

Calculate the value of Vb

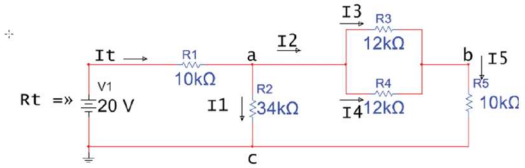

50p 100p

9.58 V	2
10.42 V	0
6.52 V	16
3.9 V	0

1 Correct +72