10:53 51%

AhaSlides

# What is a disadvantage of the Signed-Magnitude and Ones Complement methods compared to Twos Complement?

50p 100p

- They use more bits to represent the same range of numbers. 3
- They cannot represent zero. 2
- They have two representations for zero. 11
- They cannot represent negative numbers. 9

Submitted

Oh no, streak lost! +0

10:54 51%
dience.ahaslides.com
2

AhaSlides

# What is the maximum decimal value that can be represented by a 16-bit unsigned binary number?

50p 100p


- 1024 — 4
- 16384 — 3
- 65535 — 14
- 65536 — 4

Submitted

Correct +59

1

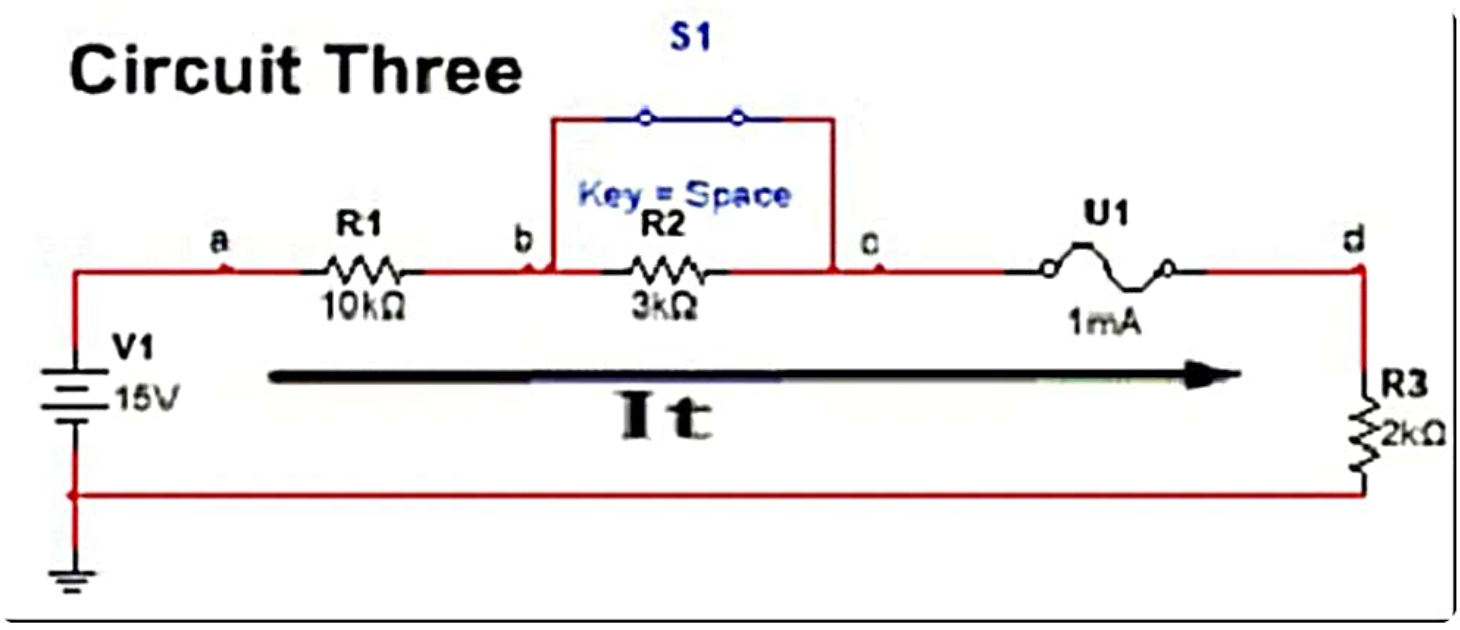With S1 closed in Circuit Three, the fuse will eventually blow (open). In that condition, it has infinite resistance and we have an OPEN circuit. What is the value of Vc when the fuse is blown?



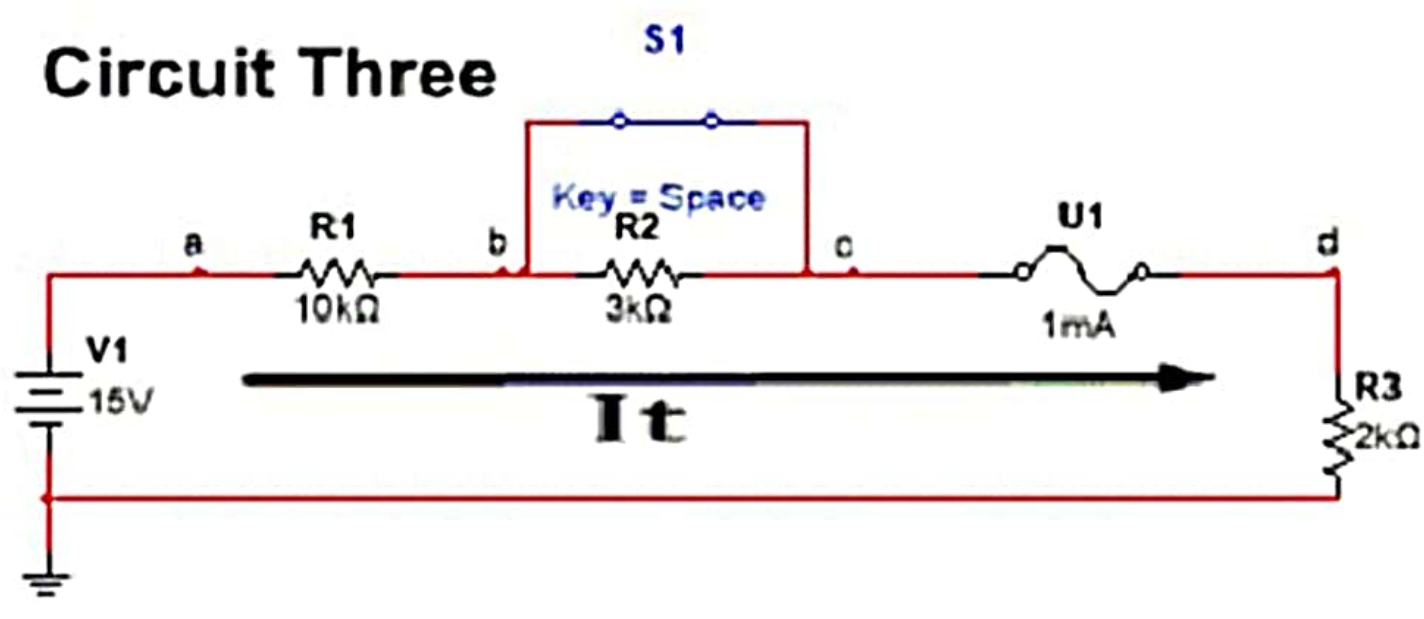

50p 100p

- 0 V — 4
- 3.462 V — 5
- 2.813 V — 2
- 15 V — 8

1 Correct +53

11:25 48%
AnaSlides

# With S1 closed in Circuit Three, the fuse will eventually blow (open). In that condition, it has infinite resistance and we have an OPEN circuit. What is the value of It when the fuse is blown?




50p 100p


- 1.145 mA — 2
- 0 A — 13
- 11.54 mA — 1
- 1.154 mA — 1

2
Two in a row! +65

11:26 48%

AhaSlides
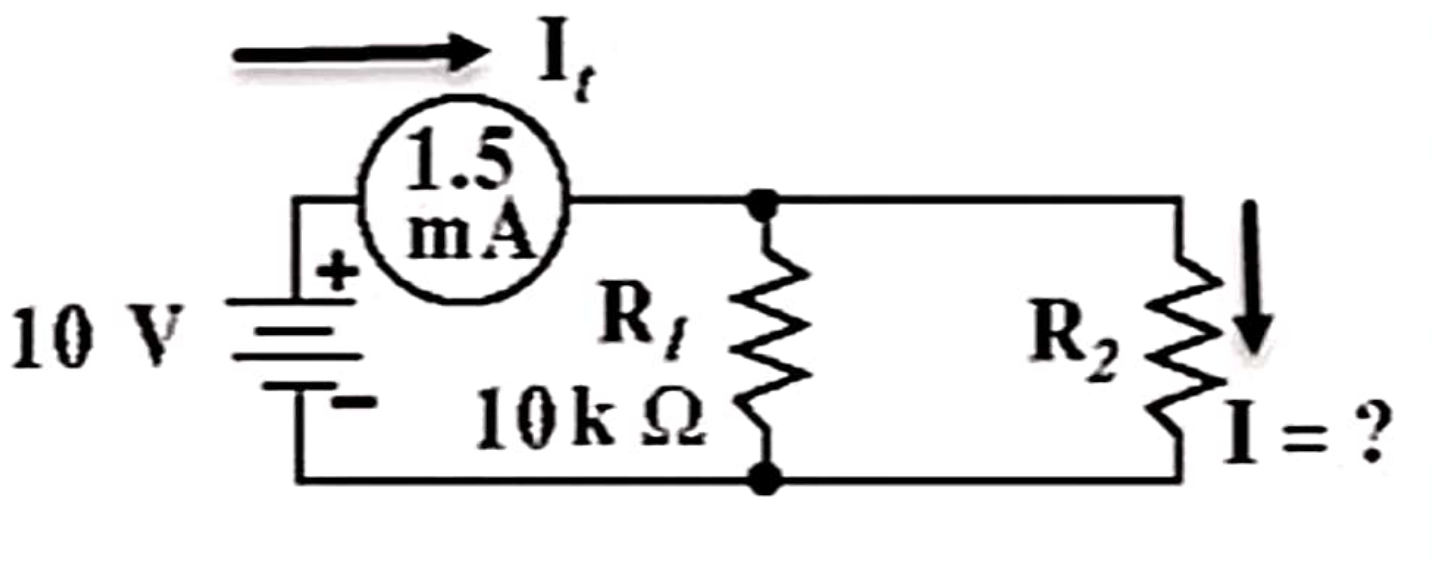
# Given the circuit, what is the current flowing through R2?




50p 100p


- 5.0 mA
- 1.0 mA
- 1.5 mA
- 0.5 mA

Submitted

11:27 48%

AhaSlides
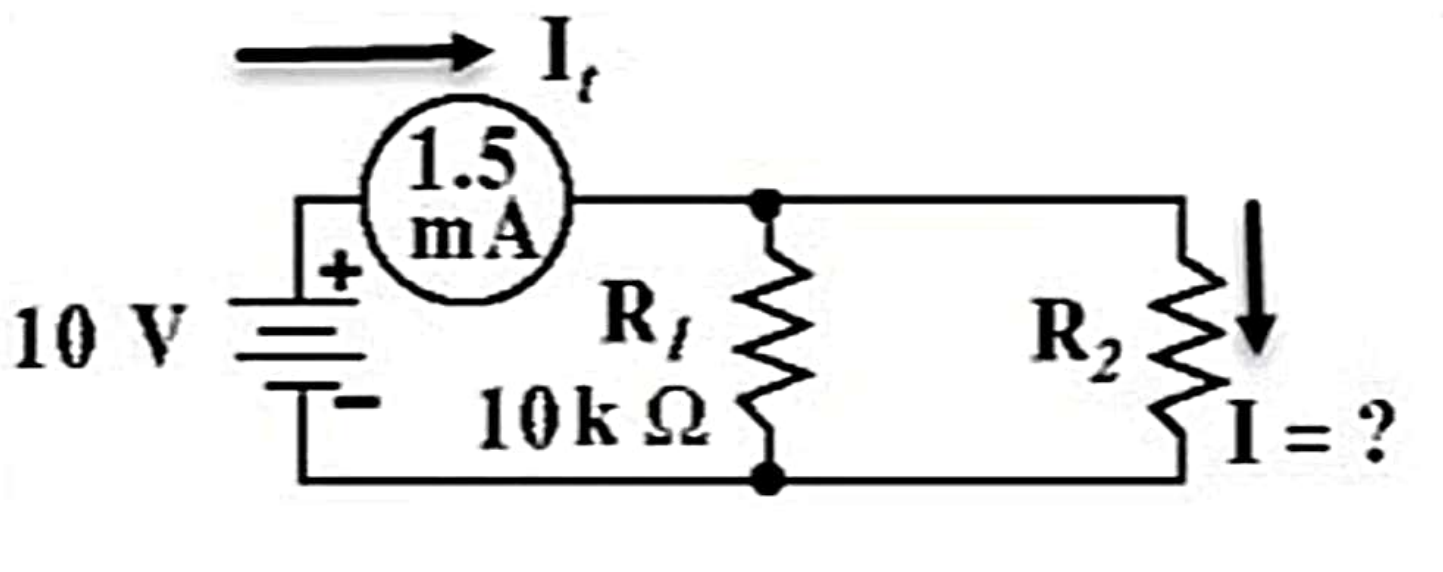
# Given the circuit, what is the current flowing through R2?




50p 100p

| | |
|---|---|
| 5.0 mA | 0 |
| 1.0 mA | 2 |
| 1.5 mA | 6 |
| 0.5 mA | 11 |


Submitted

3 That's three! +76

11:29 48%

AhaSlides
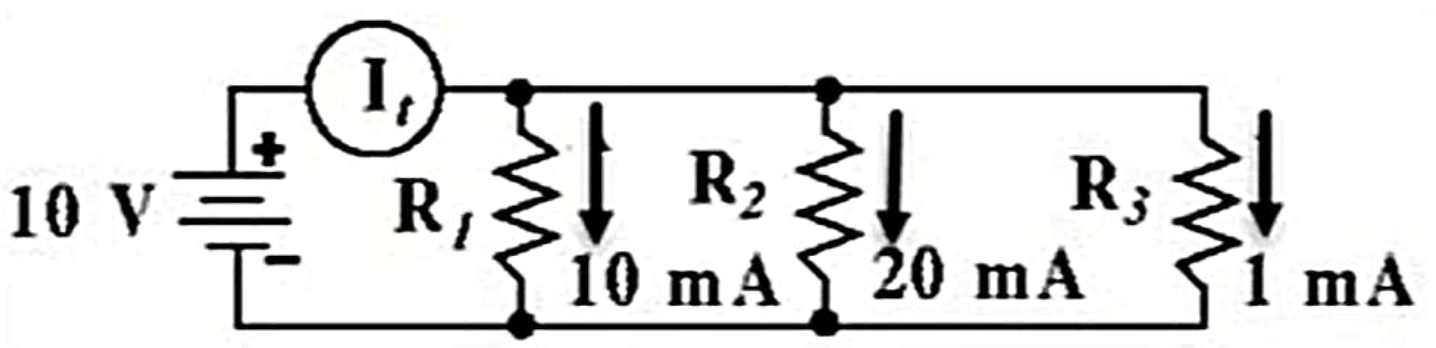
# Given the circuit, find the total power.




50p 100p

0.3 W 3

310 mW 13

310 µW 2

0.125 W 0


Submitted

4 Fantastic Four! +70

11:30 48%

AhaSlides
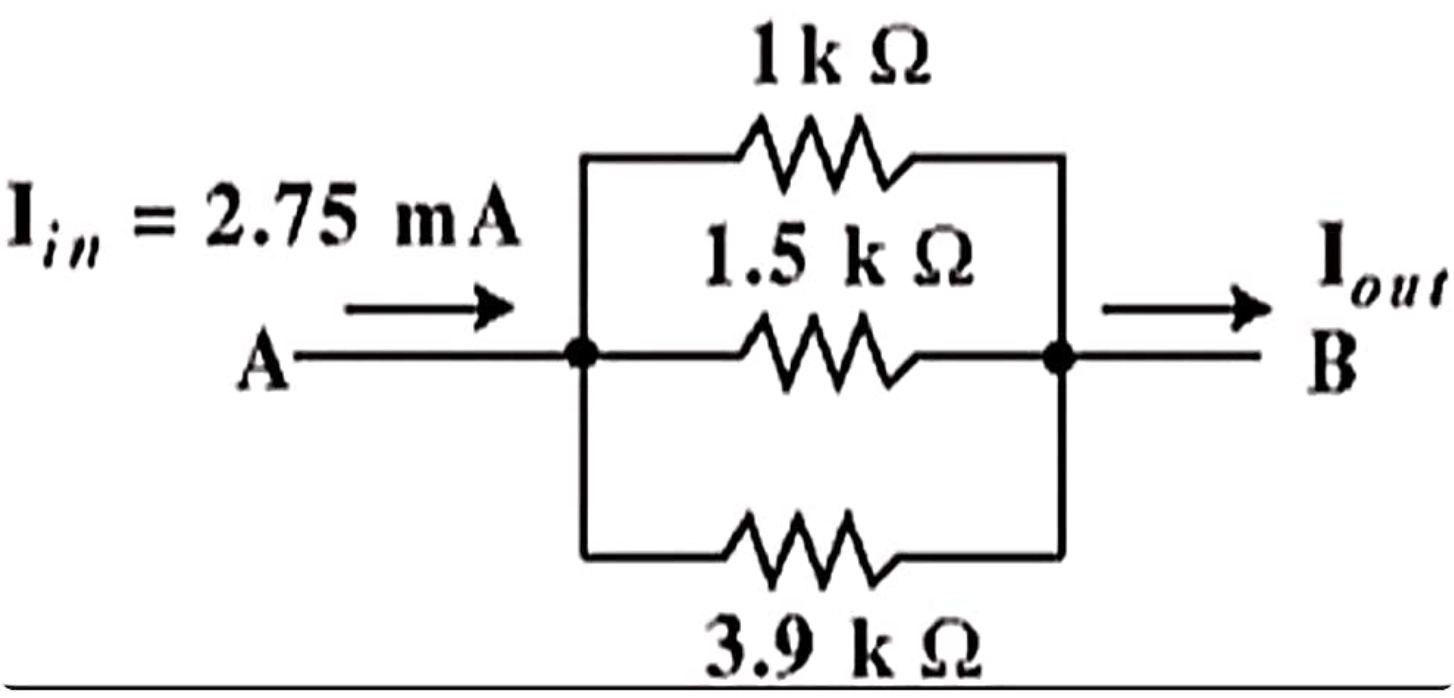
# Given the circuit, what is the output current (Iout)?




50p 100p


- [ ] 2.75 mA
- [ ] 0.916 mA
- [ ] 1.25 mA
- [ ] 0.01 A

Submitted

11:31 48%

AhaSlides
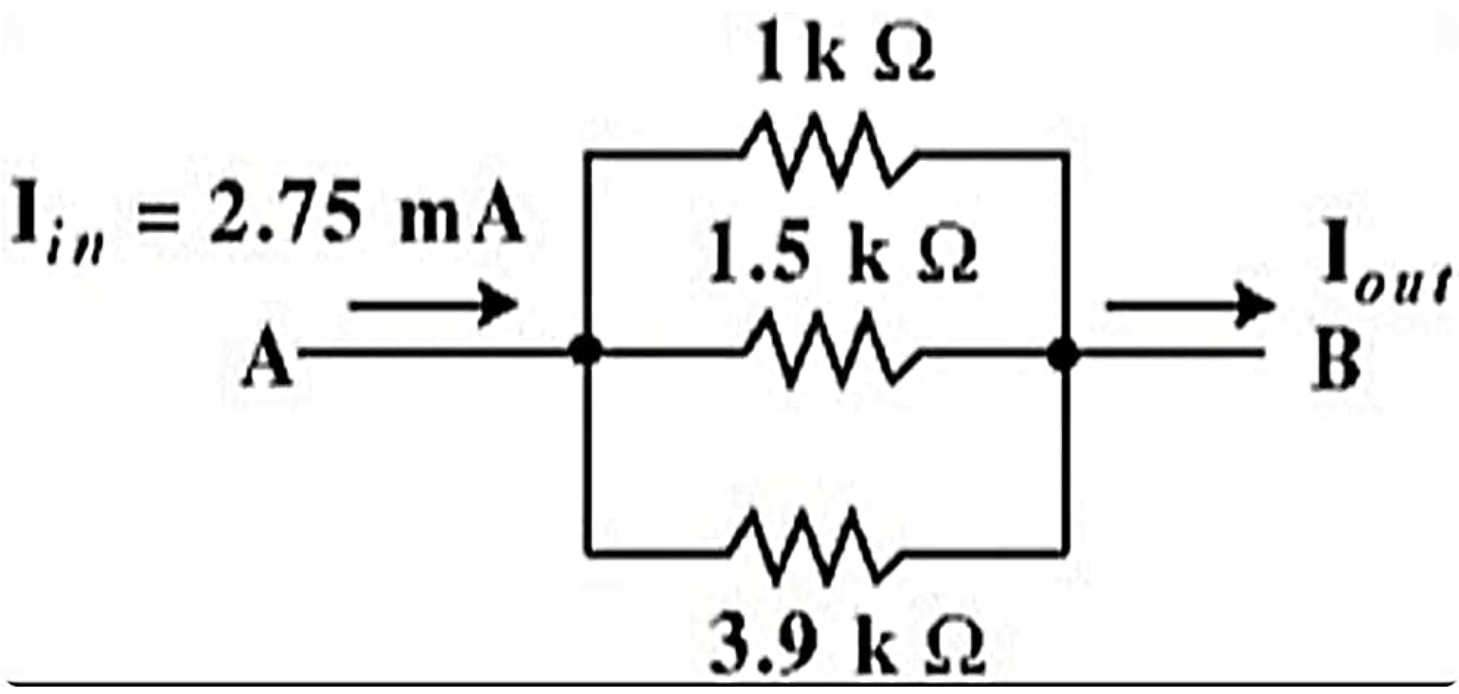
# Given the circuit, what is the output current (Iout)?




50p 100p

- ✓ 2.75 mA — 12
- ✗ 0.916 mA — 3
- ✗ 1.25 mA — 2
- ✗ 0.01 A — 1

Submitted

5 Amazing! +92

11:33 47%
dience.ahaslides.com
AhaSlides

# A series circuit consists of three resistors with values of 1.1 kΩ, 4.4 kΩ, and 2.5 kΩ across a 30 V source. The current through the 2.5 kΩ resistor is

50p 100p

- ✗ 2.24 mA — 0
- ✓ 3.75 mA — 18
- ✗ 3.75 A — 1
- ✗ 2.24 µA — 0


Submitted

Oh no, streak lost! +0

11:34 47%

AhaSlides
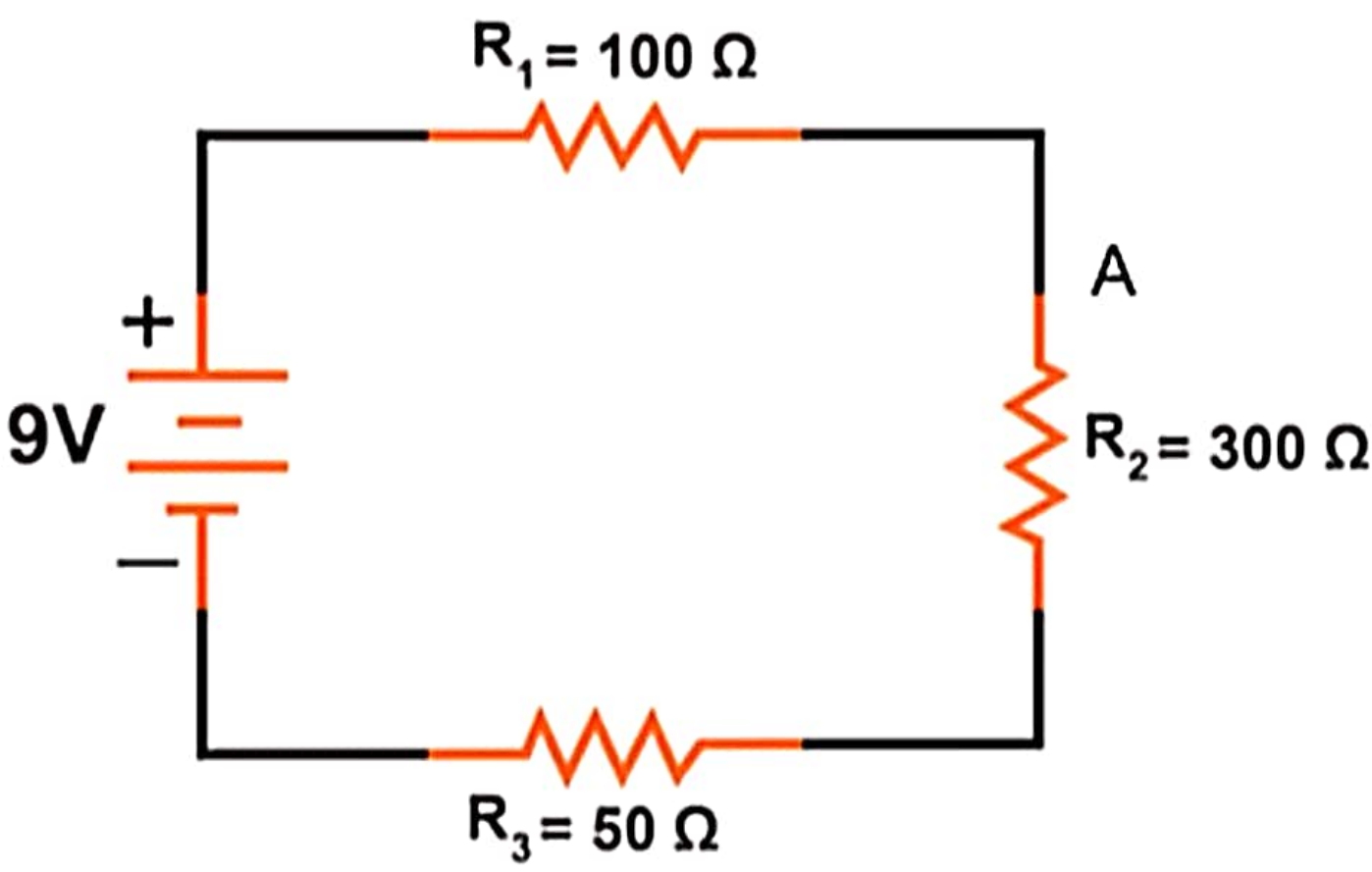
# In the series circuit shown, if R2 is open-circuited, what would the voltage at point A be?





50p 100p

- 9V
- 0V
- 7V
- 2V

Submitted
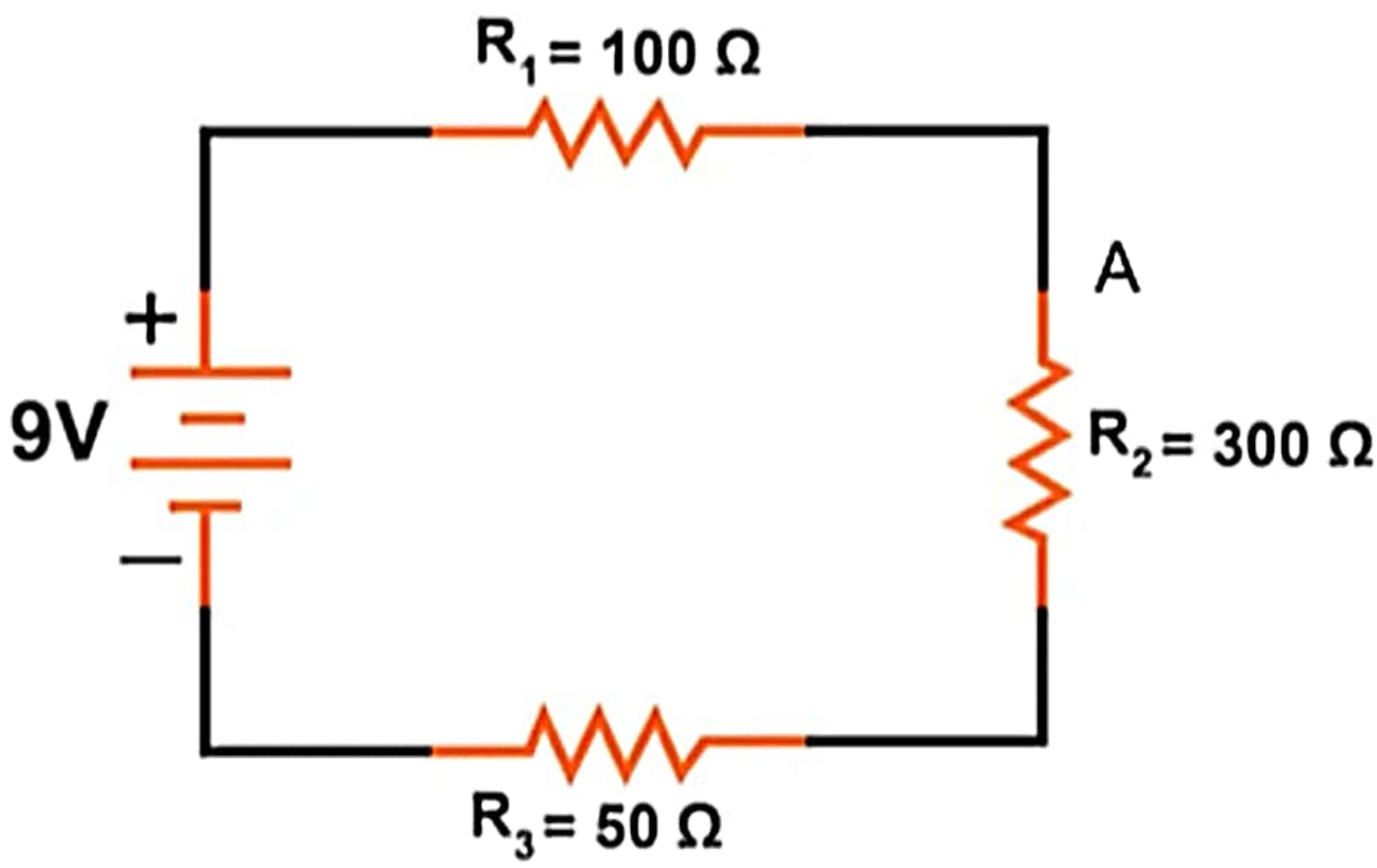
# In the series circuit shown, if R2 is open-circuited, what would the voltage at point A be?




50p 100p


- 9V — 14
- 0V — 4
- 7V — 0
- 2V — 0

1

Correct +82

11:36 47%
dience.ahaslides.com 2
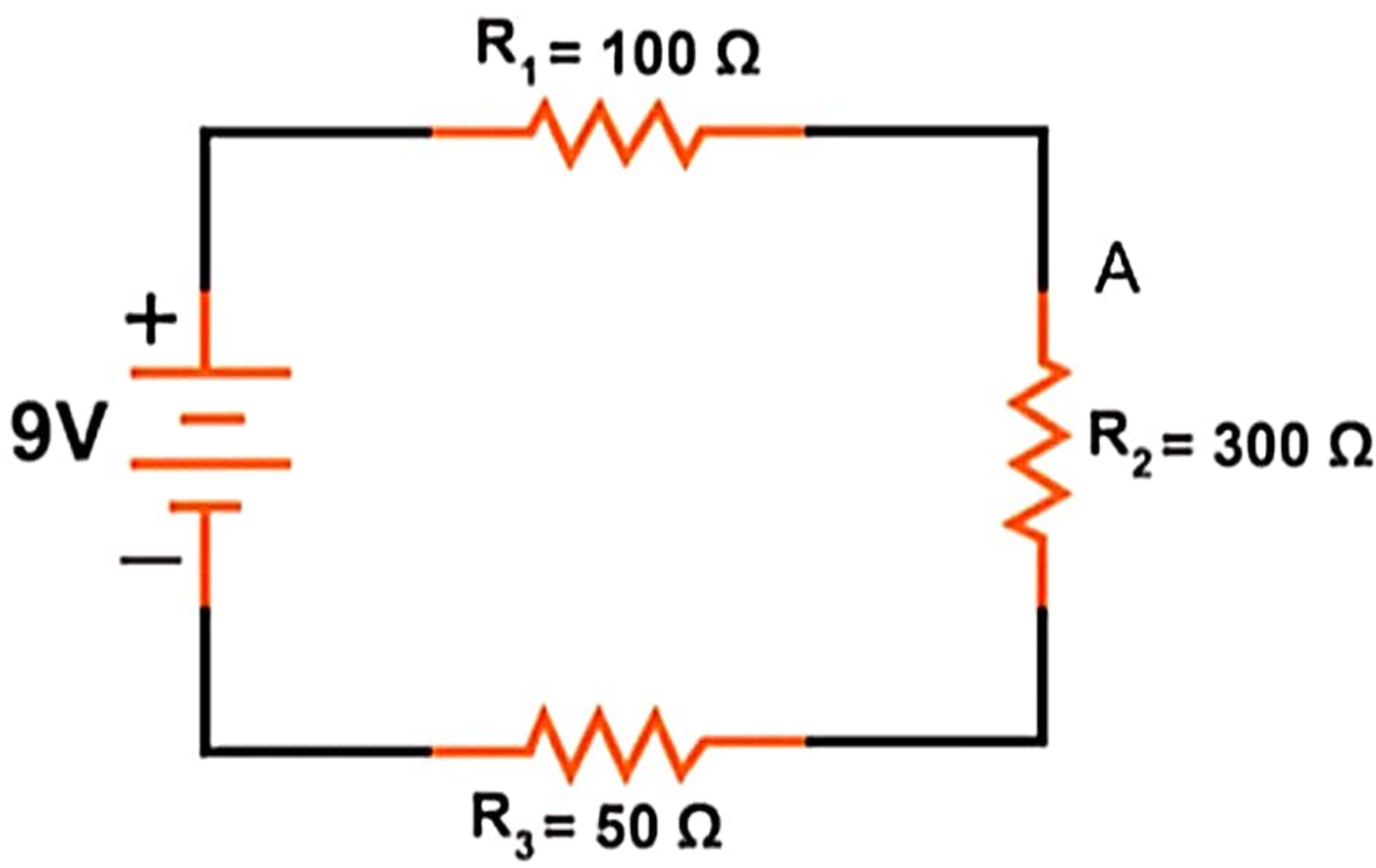
# In the series circuit shown, if R2 is short-circuited, what would the voltage at point A be?




50p 100p


- 9V — 8
- 7V — 0
- 6V — 5
- 3V — 4

Oh no, streak lost! +0

11:38 47%

AhaSlides
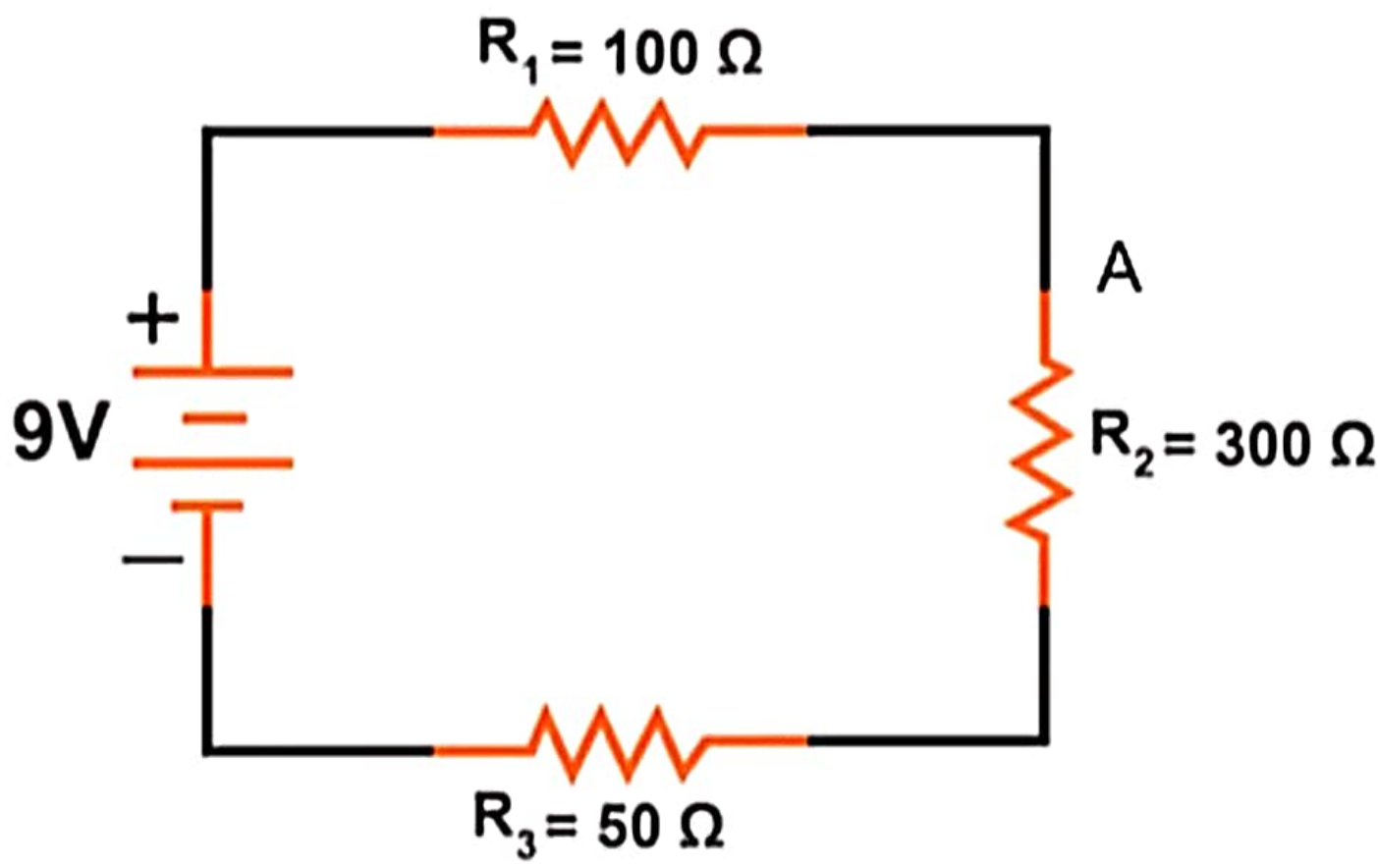
# In the series circuit shown, if $R_1$ is open-circuited, what would the voltage at point A be?




50p 100p


- 9V
- 0V
- 7V
- 2V

Submitted

11:40 47%

AhaSlides
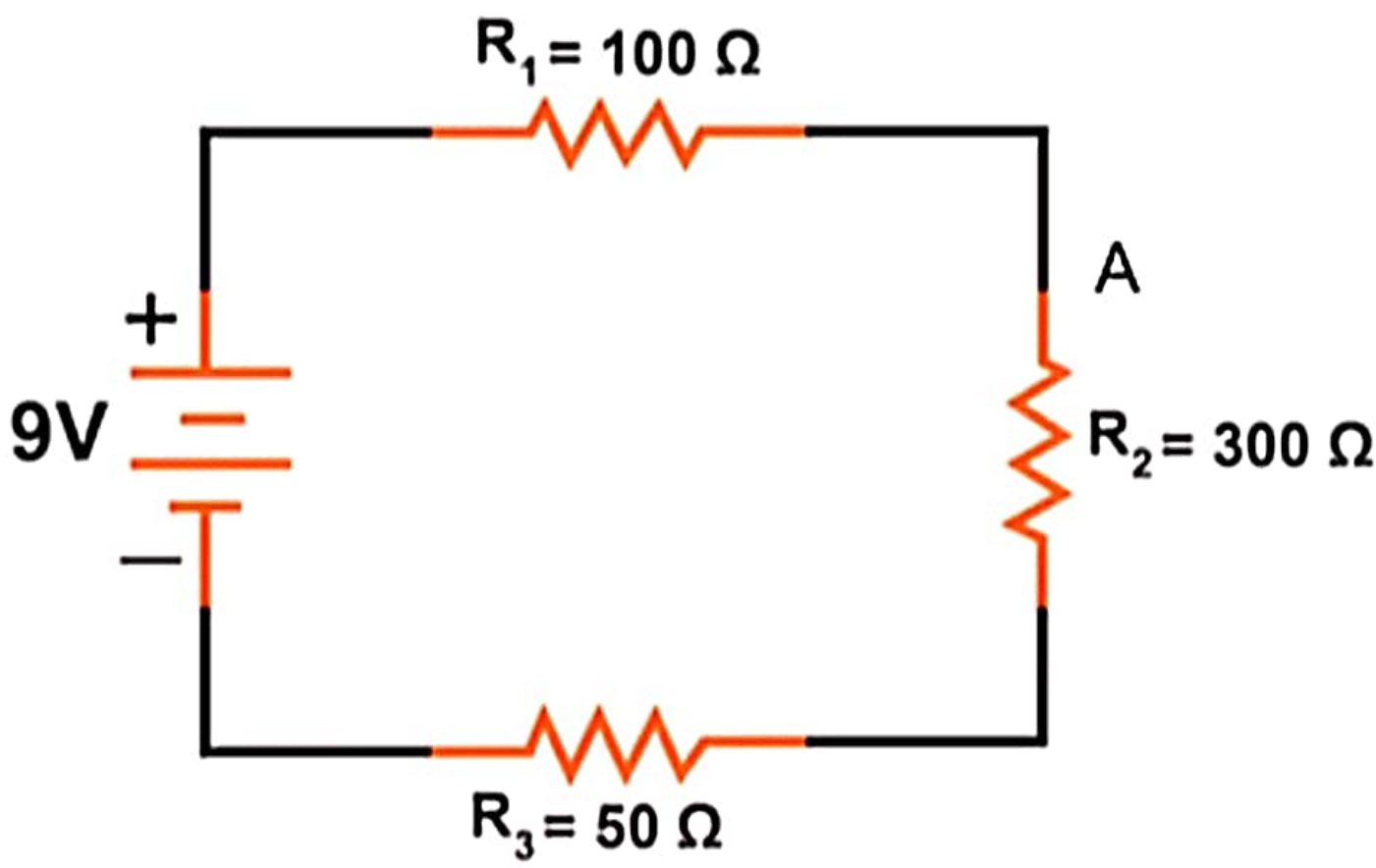
# In the series circuit shown, if $R_1$ is short-circuited, what would the voltage at point A be?



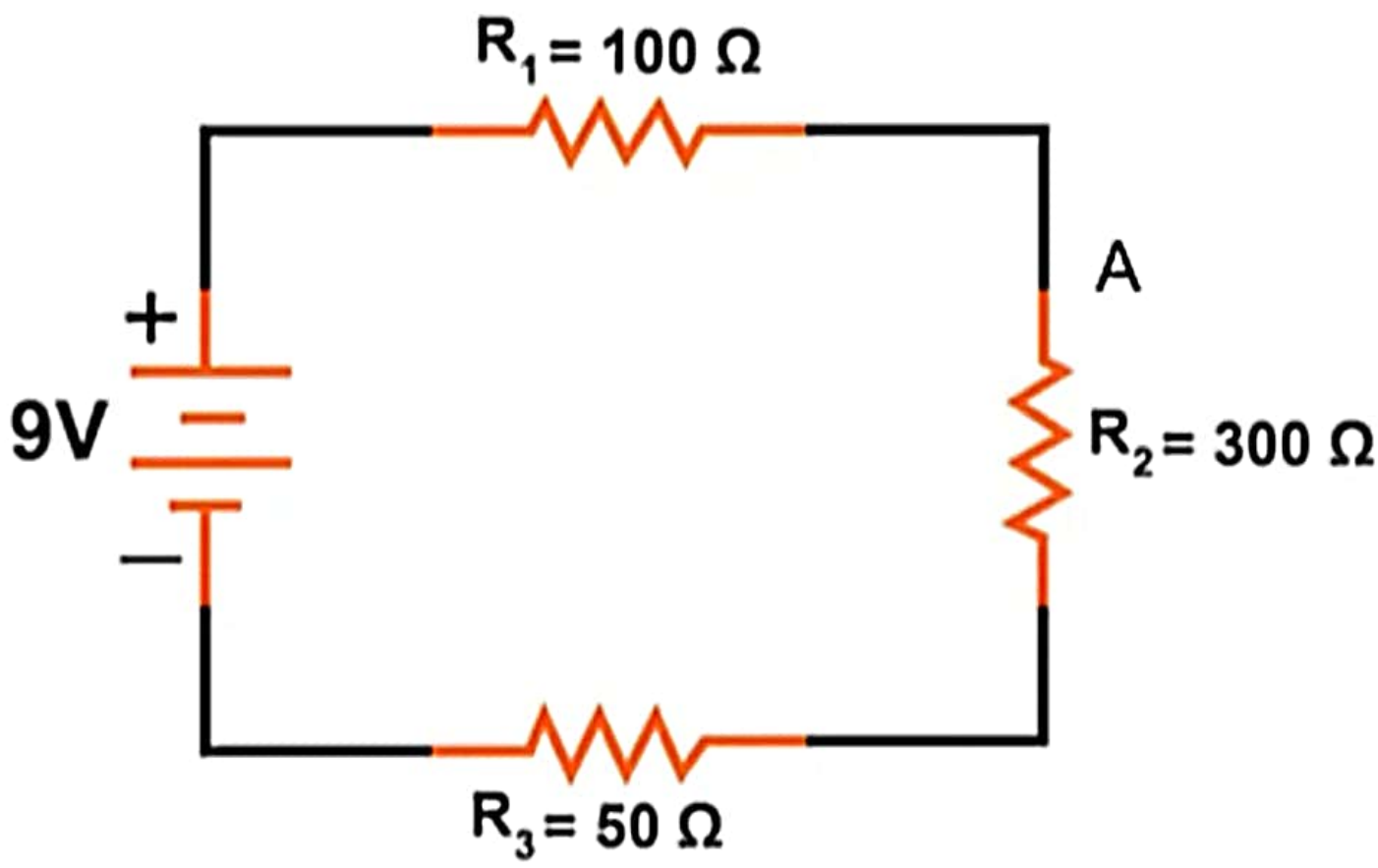

50p 100p

- 9V
- 0V
- 7V
- 2V

Submitted

11:41 46%
AhaSlides

# In the series circuit shown, if R3 is short-circuited, what would the voltage at point A be?



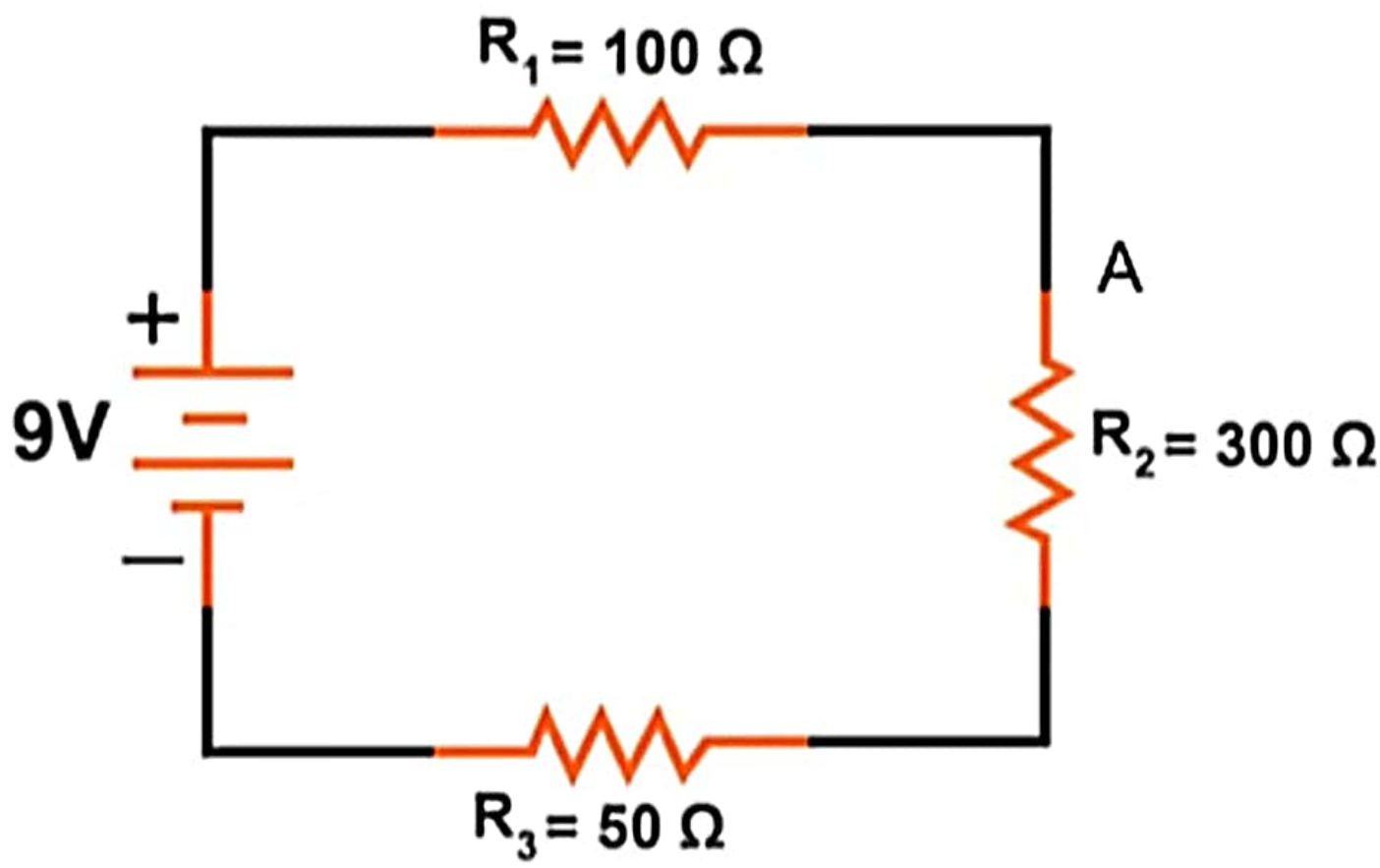

50p 100p

- ✗ 7V — 1
- ✗ 3V — 1
- ✓ 6.75V — 11
- ✗ 2.25V — 3

Oh no, streak lost! +0

11:43 46%

# In the series circuit shown, if R3 is open-circuited, what would the voltage at point A be?




50p 100p

- 0V — 8
- 9V — 6
- 6.75V — 1
- 7V — 1

Submitted

Incorrect +0